

## DIGITAL ELECTRONICS (14B11EC317)

### Tutorial-2

#### **Q1** For the following Boolean function:

$$F = xy'z + x'y'z + w'xy + wx'y + wxy$$

- Obtain the truth table.
- Draw the logic diagram using the original Boolean function.
- Use Boolean algebra to simplify the function to minimum number of literals.
- Draw the logic diagram from the simplified expression.

Sol.  $F = Y'Z + XY + WY$

#### **Q2** Minimize the following Boolean expression using laws of Boolean algebra:

(i)  $F(A,B,C) = ABC + A'B + ABC' + AC$

Sol.  $F = B + AC$

(ii)  $F(A,B,C) = A'C' + ABC + AC' + AB'$

Sol.  $F = A + C'$

(iii)  $F(A,B,C,D) = (BC' + A'D)(AB' + CD')$

Sol.  $F = 0$

#### **Q3** Express the following Boolean function in canonical sum form:

(i)  $F(A,B,C,D) = B'D + A'D + BD$

(ii)  $F(A,B,C) = BC + AB + C$

(iii)  $F(A,B,C) = (AB + C)(B + AC)$

(iv)  $F(A,B,C,D) = (A' + B')(C' + D')(B' + D)$

#### **Q4** Express the following Boolean function in canonical product of sum form:

(i)  $F(A,B,C,D) = B'D + A'D + BD$

(ii)  $F(A,B,C) = BC + AB + C$

(iii)  $F(A,B,C) = (AB + C)(B + AC)$

(iv)  $F(A,B,C,D) = (A' + B')(C' + D')(B' + D)$

#### **Q5** Simplify the following Boolean expression in (a) sum of Product (b) Product of sum

(i)  $F(A,B,C,D) = \pi(1,3,5,7,12,13,14,15)$

Sol.

Sop:-  $F = A'.D' + A.B'$

POS:-  $F = (A + D')(A' + B')$

(ii)  $F(A,B,C) = \sum(0,1,2,5,7)$

Sol.

Sop:-  $F = A'.B' + A'.C' + A.C$

POS:-  $F = (A' + C)(A + B' + C')$

(iii)  $F(A,B,C,D,E) = \sum(0,1,4,5,16,17,21,25,29)$

Sol.

Sop:-  $F = y = A'.B'.D' + B'.C'.D' + A.D'.E$

POS:-  $F = (D')(A + B')(B' + E)(A' + C' + E)$