

4 - Bit Binary Counter

Experiment No. 09

Aim: To setup a '4-Bit Binary Counter' (IC 7493) and demonstration of its 'Binary Counting Sequence'.

This experiment demonstrates the 'Count Sequence' of 'Binary Numbers' and their 'Binary Coded Decimal' representation. The Binary Counter will be used in subsequent experiments to provide the input 'Binary Signals' for testing various combinational circuits. It also acquaints you how to use oscilloscope in 'Digital Electronics Laboratory'.

General Information

IC 7493 (shown below) consists of four cells called 'Flip-Flop'. These cells can be connected to count in 'Binary' or in 'BCD'.


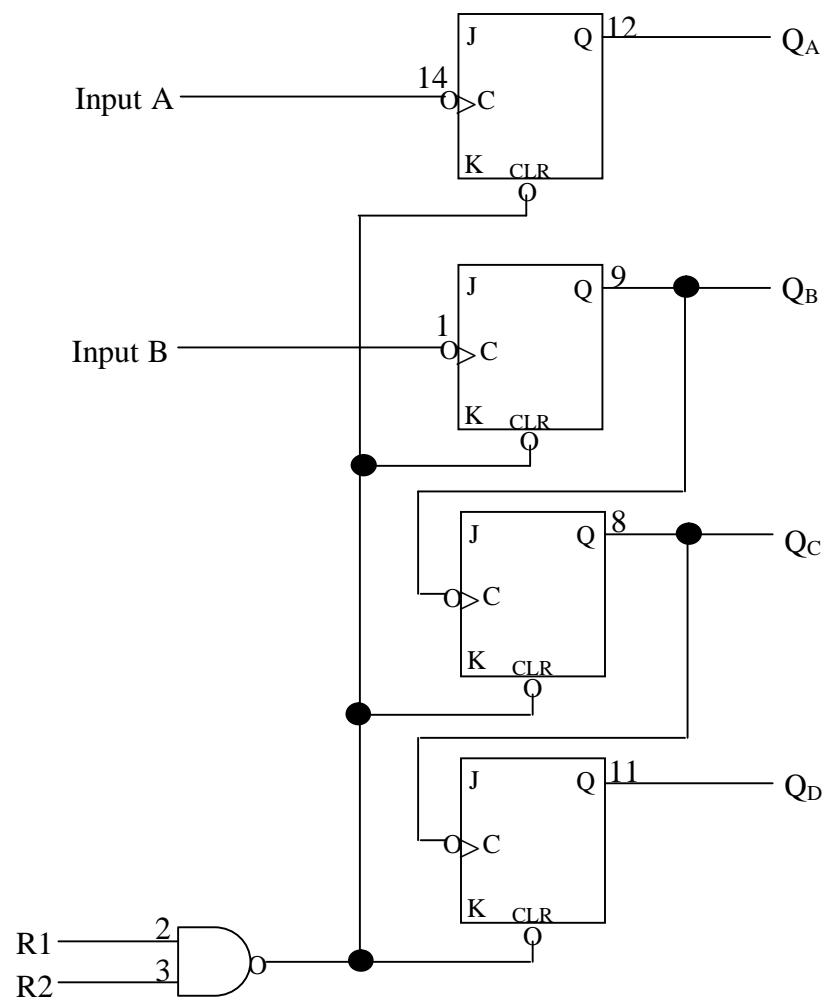


Fig. IC Type 7493 Ripple Counter 'Internal Circuit Diagram'

Activity-1(a). Binary Count

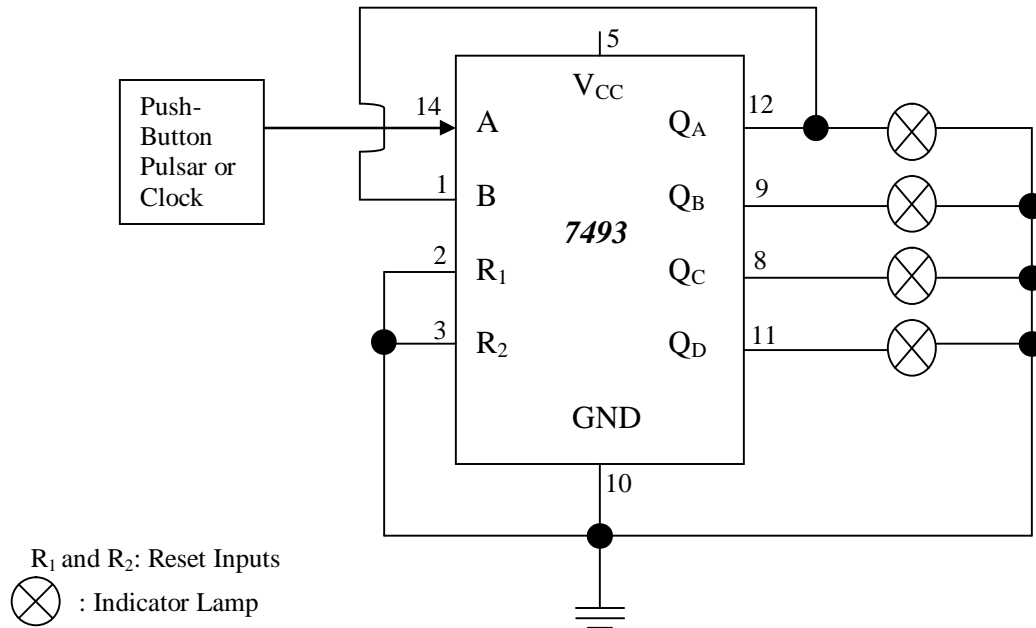Step.1. Connect the IC 7493 to operate as a '4-Bit Binary Counter' by wiring the external terminals, with Q_A as LSB and Q_D as MSB.



Step.2. Turn ON power and observe the four 'Indicator Lamps' (LEDs) by applying a 'Single Pulse' with the help of the 'Mono Pulse Generator' at pin 14.

Observations

No. of Pulses	Count Sequence			
	Q_D	Q_C	Q_B	Q_A
0				
1				
2				
3				
4				
5				
6				
7				
8				
9				
10				
11				
12				
13				
14				
15				
16				
17				

Write: The count first goes up to and then back to

Activity-1(b). Binary Count Verification

Connect the 'Clock Generator' that produces a 'Train' of 'Clock Pulse' at a 'Low Frequency' of about 'One Pulse Per Second' i.e., 1Hz by disconnecting the 'Pulsed Input' to the 'Counter'. *This will provide an 'Automatic Binary Count'*. Observe and verify, your previous results you tabulated in previous page.

Observations:

Write Comment:

Activity 2. Oscilloscope Display


Step.1. Increase the 'Clock Frequency' to 10kHz. Observe this 'Clock' output in an 'Oscilloscope'. Sketch its waveform. (*Make sure that you included at least 16 clock pulses*).

Step.2. In a 'Dual-Trace Oscilloscope' connect the output Q_A to one channel and the output of the clock to second channel. Sketch, the output Q_A with reference to clock applied.

Step.3. Repeat by observing and recording the waveforms of Q_A together with Q_B , followed by the waveforms of Q_B with Q_C and then Q_C with Q_D .

Observations

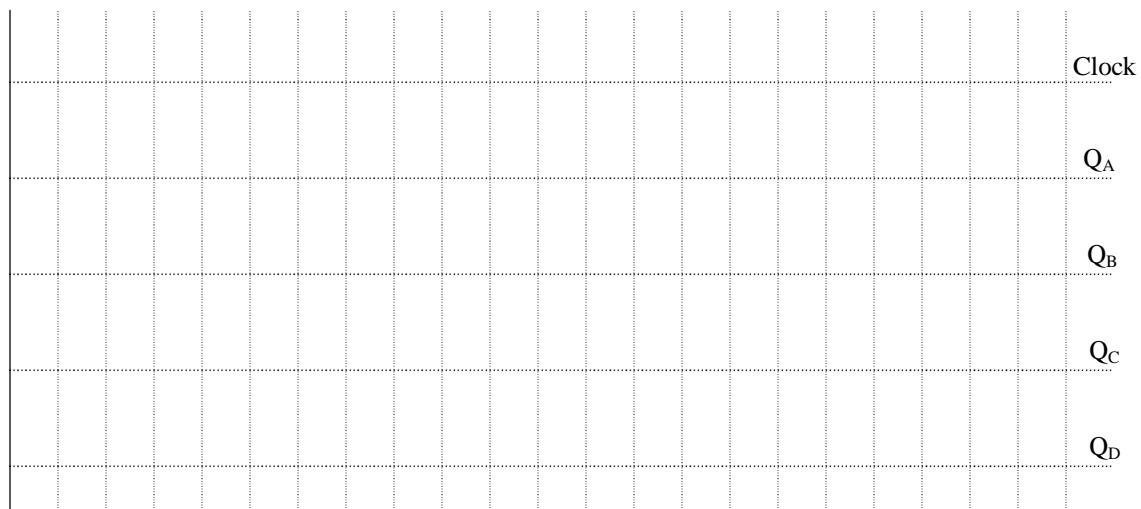Note: Your final result should be a diagram showing the 'Time Relationship' of the clock and the four outputs in one composite diagram having at least 16 clock pulses.



By observing the above waveforms, write:


1. The output of Q_A is complemented every time the clock pulse goes through a transition, i.e., from to
2. What is the relationship between clock and output Q_A , $f_{\text{clock}} = \dots\dots\dots \& f_{Q_A} \dots\dots\dots$
3. What is the relationship between outputs Q_B and Q_A , $f_{Q_B} = \dots\dots\dots \& f_{Q_A} \dots\dots\dots$
4. What is the relationship between outputs Q_C and Q_B , $f_{Q_C} = \dots\dots\dots \& f_{Q_B} \dots\dots\dots$

5. What is the relationship between outputs Q_D and Q_C , $f_{QD} = \dots\dots\dots \& f_{QC} \dots\dots\dots$

Discuss above points:

Activity-3(a). BCD Counts

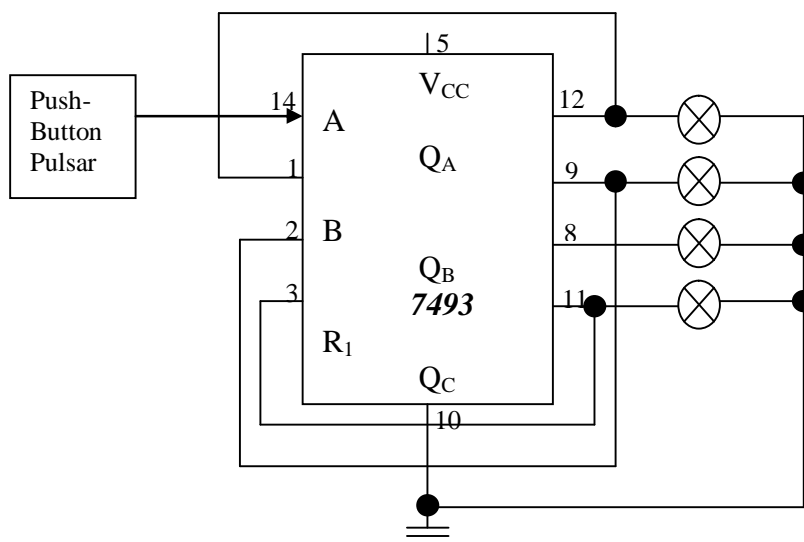The counter starts from 0 (0000) and every input pulse increments it by 1 until it reaches the count of 9 (1001). The next pulses changes the output again to 0 (0000). The BCD representation uses the binary numbers from 0000 to 1001 for representing the 'Decimal Digits' from 0 to 9. IC type 7493 can be operated as a 'BCD Counter' by making the external connections, as shown below.



Procedure

Step.1. Construct the circuit as shown above.

Step.2. Connect the input to a pulsar and the four outputs to indicator lamps (LEDs).

Observations

Input Pulses	Outputs			
	Q_A	Q_B	Q_C	Q_D
1				
2				
3				
4				
5				
6				
7				
8				
9				
10				
11				

Activity-3(b). BCD Counts(output display through seven-segment)

Step.2. Disconnect the 1Hz input clock and four outputs from the four indicator lamps/LEDs. *Step.3.* Reconnect input to a pulsar and connect outputs to a '7-Segment LED Display' by connecting Q_D as MSB and Q_A as LSB.

Observations

Activity-3(c). BCD Counts(Output observe through CRO)

Step.3. Observe and record the clock waveform and the four outputs on the oscilloscope to obtain an accurate timing diagram showing the time relationship between the clock and the four outputs.

Observations

Timing diagram for a 4-bit ripple-carry adder. The diagram shows four horizontal lines for signals: Clock, Q_A , Q_B , and Q_C . The Clock signal is a periodic square wave. Q_A and Q_B are square waves that change state on the rising edge of the Clock. Q_C is a square wave that changes state on the falling edge of the Clock. The diagram illustrates the propagation of a carry from Q_C to Q_A and Q_B .

