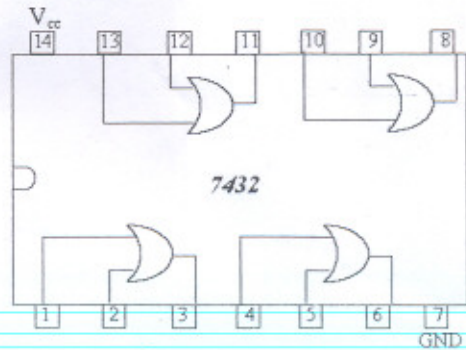


*Logic Diagram of OR gate*



*Pin-out Diagram of IC 7432*