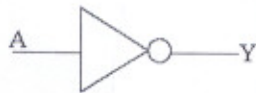
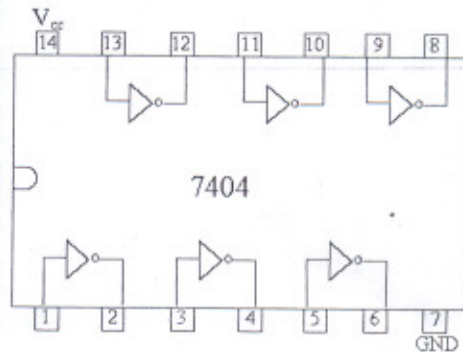


Activity-3. Implementation of Logic NOT Gate using IC 7404



*Logic Diagram of NOT gate*



*Pin-out Diagram of IC 7404*