

DEMULTIPLEXERS

Experiment No. 08

Aim: Implementation of Demultiplexure using gates and TTL ICs

Demultiplexers: The word "demultiplexure" means 'one into many'. Demultiplexing is the process of taking information from one input and transmitting the same over one of several outputs. The demultiplexure (Data-Distributor) has one input signal D , m select signals ($S_m, S_{m-1}, \dots, S_1, S_0$), and n output signals ($Y_0, Y_1, \dots, Y_{n-1}, Y_n$). The select inputs determine to which output the data input will be connected. Its block diagram is shown in Fig.1, below.

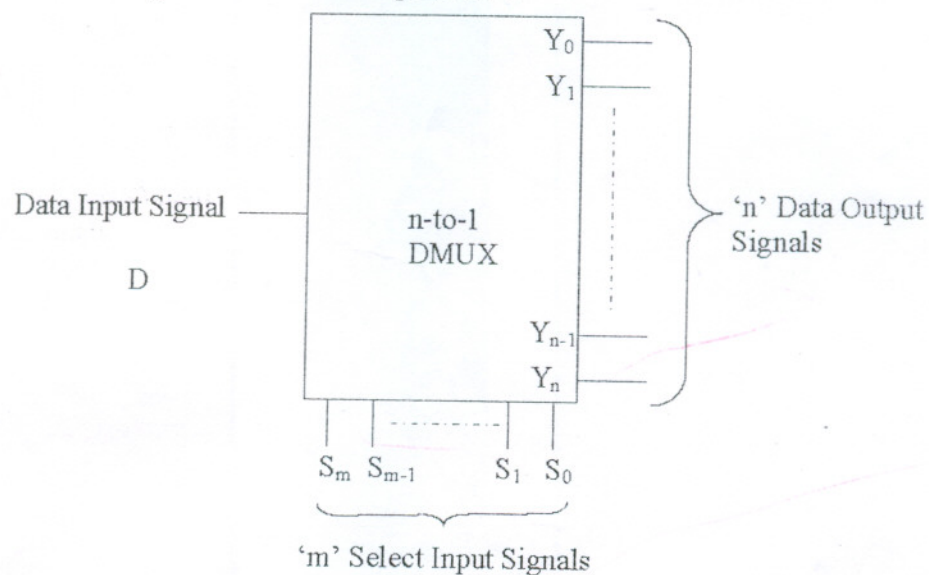


Fig.1. Block Diagram of n -to-1 DMUX.

Activity 1. 1-to-2 line Demultiplexer

A 1-to-2 DMUX has one data input line, one select line, and two output lines. Its logic symbol is shown in Fig.2, below.

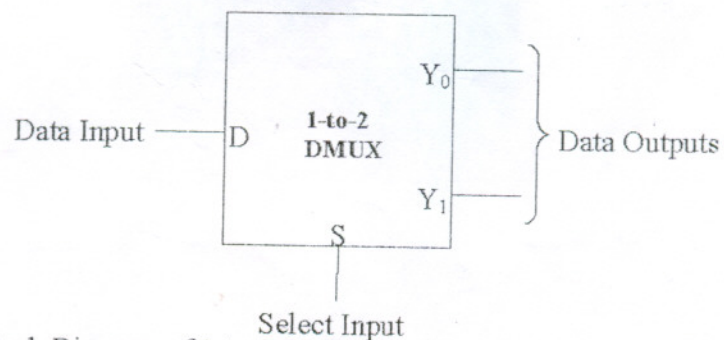


Fig.2. Block Diagram of 1-to-2 DMUX

Logic Diagram:

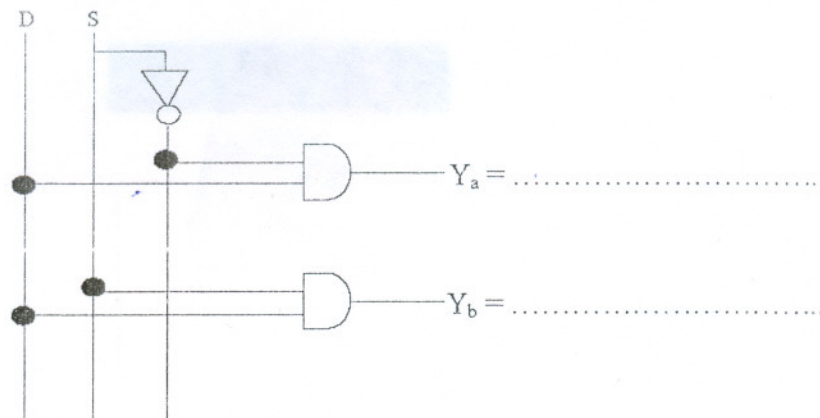


Fig.3. Logic Diagram

Procedure

Step.1. Construct the circuit shown in Fig.3.

Step.2. Apply the data input signal (D), select input signal (S), and record the outputs (Y_0 and Y_1).

Observations: Truth-Table

Select Inputs	Data Input	Outputs	
S	D(0/1)	Y_0	Y_1
0	D(0/1)		
0	D(0/1)		
1	D(0/1)		
1	D(0/1)		

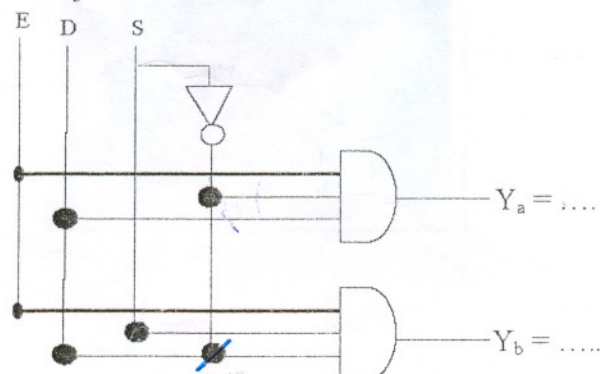
Activity 2. Implementation of 1-to-2 line DMUX with Enable / Disable input

Fig.4. Logic Diagram of 1-to-2 line DMUX with enable/disable input

Connect an extra Enable signal 'E' to the 1-to-2 DMUX, as shown in Fig.4.

Observations: Truth-Table

Enable Input	Select Inputs	Data Input	Outputs	
E	S	D(0/1)	Y_0	Y_1
1	0	D(0/1)		
0	0	D(0/1)		
1	1	D(0/1)		
0	1	D(0/1)		

Write:

1. When Enable Input is HIGH, the Output of the DMUX is(Enabled / Disabled).
2. When Enable Input is LOW, the Output of the DMUX is (Enabled/Disabled).

Activity 3. 1-to-4 Demultiplexer

A 1-to-4 DMUX has a single data input (D), two select inputs (S1 and S2), and four outputs (Y_0, Y_1, Y_2, Y_3). Its logic symbol is shown in Fig.4, below.

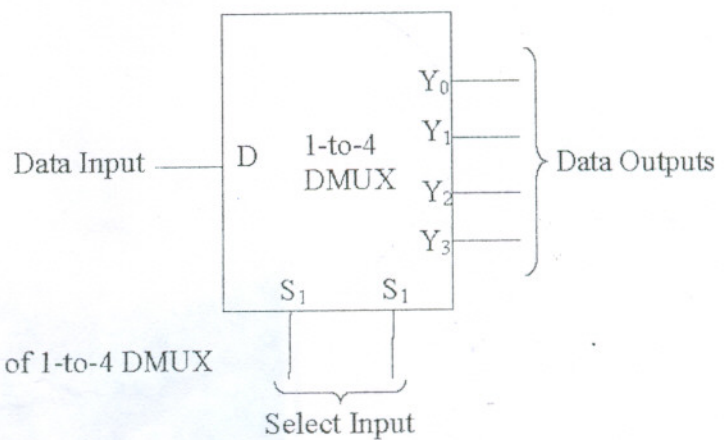


Fig.5. Block Diagram of 1-to-4 DMUX

1-to-4 Demultiplexer Using IC 74139

The logic symbol of IC 74139 (Dual 1-to-4 Decoder / Demultiplexer) is shown in Fig.6, below.

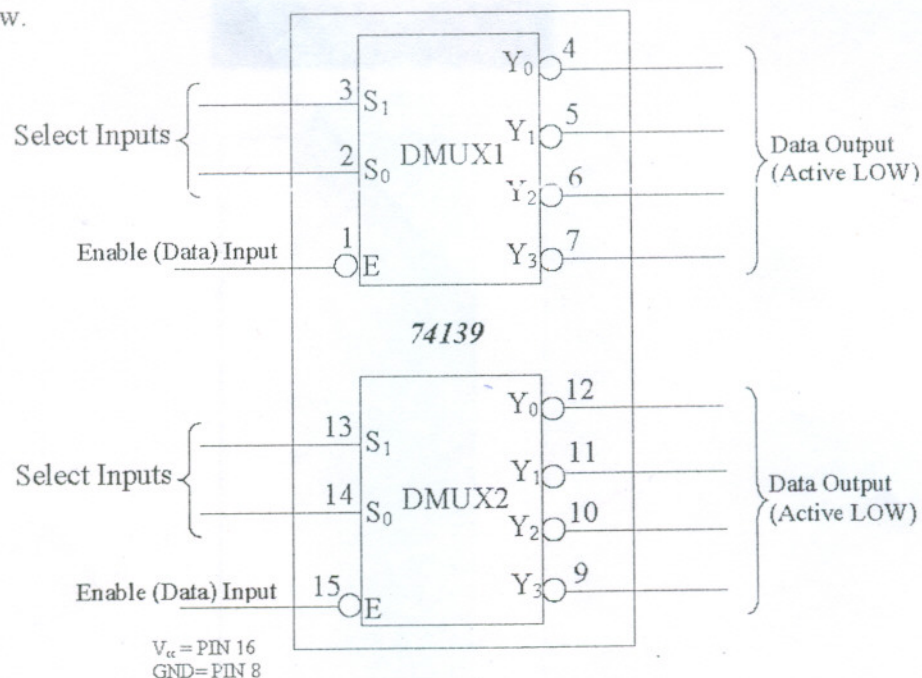


Fig.6.

Procedure:

- Step.1. Choose any DMUX (say DMUX1) to perform the experiment.
- Step.2. Make the proper connections of the Data Input, Select Input, and Outputs.
- Step.3. Apply the Data Signal, and Select Signals.
- Step.4. Observe and record the outputs.

Observations: Truth-Table

Data Input	Select Inputs		Outputs			
D	S ₁	S ₀	Y ₀	Y ₁	Y ₂	Y ₃
D(0/1)	0	0				
D(0/1)	0	1				
D(0/1)	1	0				
D(0/1)	1	0				