

BASIC LOGIC GATES

Experiment No. 01

Aim: To implement AND, OR, NOT, NAND, NOR, and XOR gates using TTL ICs.


Let inputs to a gate are A & B and Y is the output.

This experiment serves as an introduction to the 'Bread-Boards' used in the laboratory and to understand the function of various TTL ICs.

Activity-1. Implementation of Logic AND Gate using IC 7408



Logic Diagram of AND gate

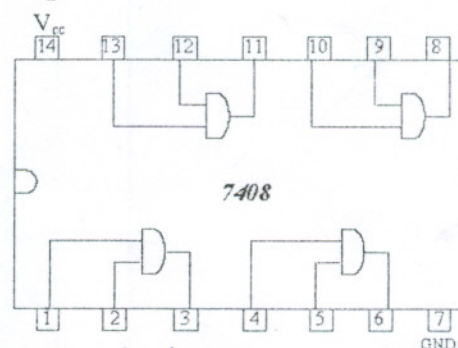

Pin-out Diagram of IC 7408

Observations

- What is the number of AND gates in the IC 7408
- Complete & Verify the 'Truth-Table' for any one of the four AND gates.

Truth-Table: 'AND Gate'


Inputs		Outputs
A	B	Y
0	0	
0	1	
1	0	
1	1	

- With the help of the above 'Truth-Table' write the 'Switching Expression's

Activity-2. Implementation of Logic OR Gate using IC 7432



Logic Diagram of OR gate

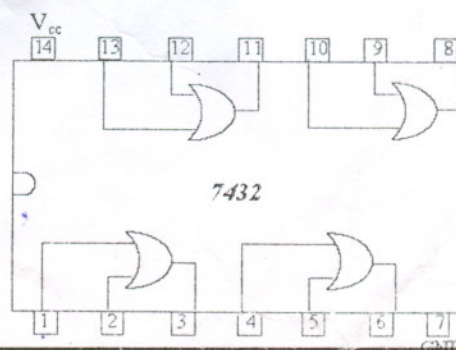

Pin-out Diagram of IC 7432

Observations


- (i) What is the number of OR gates in the IC 7432
- (ii) Complete & Verify the 'Truth-Table' for any one of the four OR gates.

Truth-Table: 'OR Gate'


Inputs		Outputs
A	B	Y
0	0	
0	1	
1	0	
1	1	

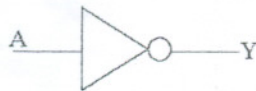- (iii) With the help of the above 'Truth-Table' write the 'Switching Expression's

Activity-3. Implementation of Logic NOT Gate using IC 7404



Logic Diagram of NOT gate

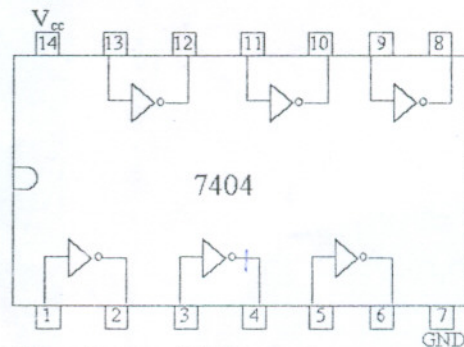

Pin-out Diagram of IC 7404

Observations


- (i) What is the number of NOT gates in the IC 7404
- (ii) Complete & Verify the 'Truth-Table' for any one of the six NOT gates.

Truth-Table: 'NOT Gate'


Inputs	Outputs
A	Y
0	
1	

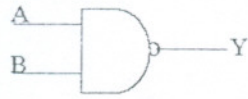- (iii) With the help of the above 'Truth-Table' write the 'Switching Expression's

Activity-4. Implementation of Logic NAND Gate using IC 7400



Logic Diagram of NAND gate

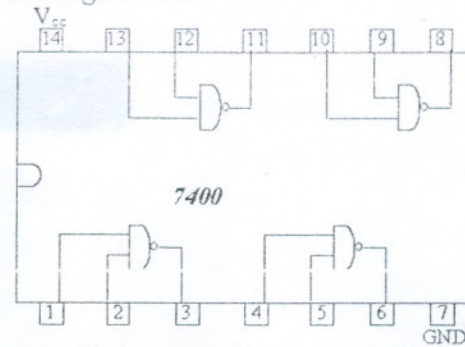

Pin-out Diagram of IC 7400

Observations


- (i) What is the number of NAND gates in the IC 7400
- (ii) Complete & Verify the 'Truth-Table' for any one of the four NAND gates.

Truth-Table: 'NAND Gate'


Inputs		Outputs
A	B	Y
0	0	
0	1	
1	0	
1	1	

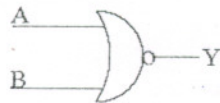- (iii) With the help of the above 'Truth-Table' write the 'Switching Expression's

Activity-5. Implementation of Logic NOR Gate using IC 7402



Logic Diagram of NOR gate

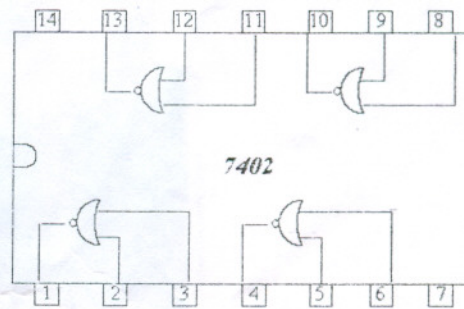

Pin-out Diagram of IC 7402

Observations


- (i) What is the number of NOR gates in the IC 7402
- (ii) Complete & Verify the 'Truth-Table' for any one of the four NOR gates.

Truth-Table: 'NOR Gate'


Inputs		Outputs
A	B	Y
0	0	
0	1	
1	0	
1	1	

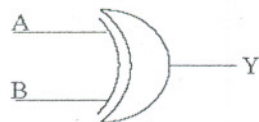(iii) With the help of the above 'Truth-Table' write the 'Switching Expression's

Activity-6 Implementation of Logic XOR Gate using IC 7486



Logic Diagram of XOR gate

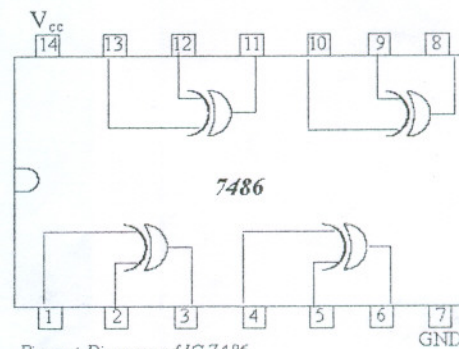

Pin-out Diagram of IC 7486

Observations

- What is the number of XOR gates in the IC 7486
- Complete & Verify the 'Truth-Table' for any one of the four XOR gates.

Truth-Table: 'XOR Gate'

Inputs		Outputs
A	B	Y
0	0	
0	1	
1	0	
1	1	

(iii) With the help of the above 'Truth-