


## Combinational Circuit

### Experiment No. 2

**Aim:** Implementation of combinational circuits using MSI Logic

Construct and identify the function performed by the 'Block Diagram' shown below.

**Activity-1.** Block Diagram-1

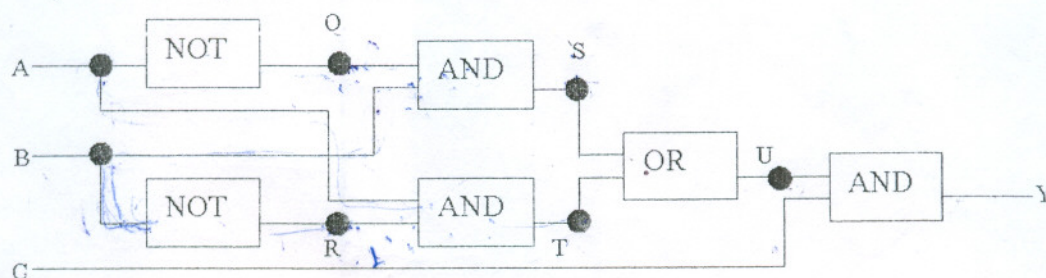

**Observations**

(i) When C is at Logic '0'

Inputs			Intermediate Outputs					Outputs
A	B	C	Q	R	S	T	U	Y
0	0	0						
0	1	0						
1	0	0						
1	1	0						


(ii) When C is a Logic '1'

Inputs			Intermediate Outputs					Outputs
A	B	C	Q	R	S	T	U	Y
0	0	1						
0	1	1						
1	0	1						
1	1	1						

(iii) By observing the 'Truth-Tables' write the name of the operation (when C is logic '1') finally performed by the 'Block Diagram.1' shown above. ....

(iv) What is the significance of the input C in the above circuit .....

**Activity-2. Block Diagram-2**

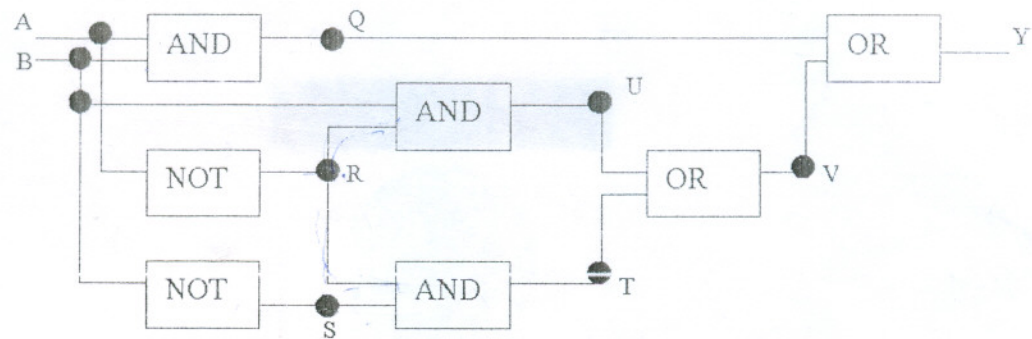


**Observations**

Inputs		Intermediate Outputs						Outputs
A	B	Q	R	S	T	U	V	Y
0	0							
0	1							
1	0							
1	1							

By observing the 'Truth-Tables' write the name of the operation finally performed by the 'Block Diagram-2' shown above .....

**Exercise.9. Block Diagram-3**

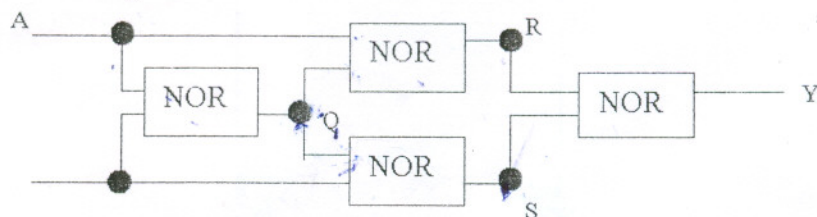

**Observations**

Inputs		Intermediate Outputs			Outputs
A	B	Q	R	S	Y
0	0				
0	1				
1	0				
1	1				

(i) By observing the 'Truth-Tables' write the name of the operation finally performed by the 'Block Diagram-3' shown above. ....

(ii) Suggest a modification in the circuit shown above to get an 'Logic XOR' function  
.....  
.....