

Activity 2 4-Bit Bi-directional Universal Shift Register

The IC 74195 is a 4-Bit Bidirectional Universal Shift register. It may be used in Serial-Serial, Shift-Left, Shift-Right, serial-Parallel, Parallel-Serial, and Parallel-Parallel Data register transfer. Its connection diagram is shown in the Fig.3, below.

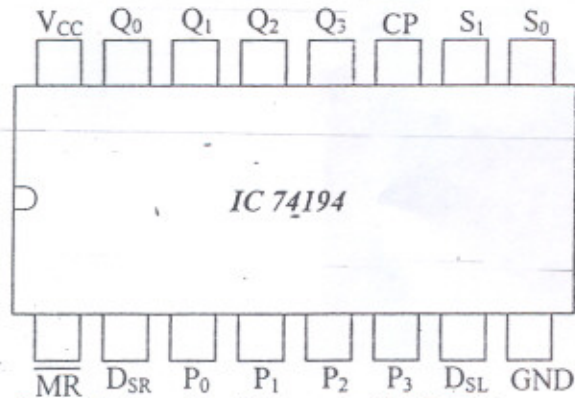


Fig.3. Connection Diagram of IC 74194

PIN Names:

S₁, S₀ : Mode Control Inputs

P₀ – P₃ : Parallel Data Inputs

D_{SR} : Serial (Shift Right) Data Input

D_{SL} : Serial (Shift Left) Data Input

CP : Clock Input

MR : Master Reset

Q₀ – Q₃ : Parallel Outputs