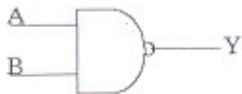
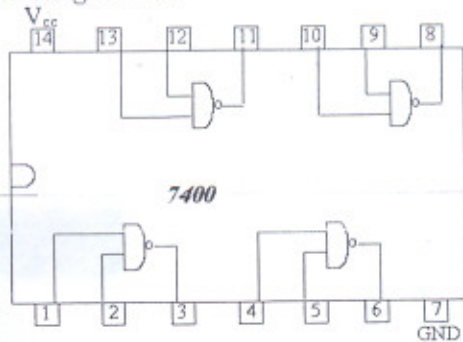


Activity-4. Implementation of Logic NAND Gate using IC 7400



Logic Diagram of NAND gate



Pin-out Diagram of IC 7400

Observations